

ECE 551

Homework #2

Due: Mon Oct 4th @ 11:55PM

Please Note: For this homework, you *must*:

- Use informative module/signal/port names.
- 1) (20pts) Dataflow (RTL) warmup...a 16-bit left shifter/rotator. Using dataflow/RTL verilog implement a shifter/rotator (**lshift_rot.sv**) capable of performing left shifts or rotates on a 16-bit input (**src[15:0]**). The shift amount can be anywhere from 0 to 15-bits, and is specified by a 4-bit input (**amt[3:0]**). The result goes to a signal called **res[15:0]**. You are **not** allowed to use the << or <<< operator. Write a testbench (**lshift_rot_tb.sv**) to verify its operation. This testbench should be self-checking. (Please ensure reasonably comprehensive coverage with stimulus. i.e. cover multiple 16-bit quantities for both shifts and rotates and for multiple shift amounts).

Signal Name:	Dir:	Description:
src[15:0]	in	Input vector to be shifted/rotated
rot	in	If asserted rotate instead of shift
amt[3:0]	in	Specifies shift amount 0 to 15
res[15:0]	out	Result of shift

Submit:


lshift_rot.sv → verilog of shifter
lshift_rot_tb.sv → testbench
lshift_waves.jpg → capture of waveforms from your testbench proving you ran it.

This problem started as in class exercise (Ex06) on Weds Sept 22nd

- 2) (20pts) See exercise06 for more detailed description.

Signal:	Dir:	Description:
error[11:0]	in	12-bit signed error term MEMs gyro.
P_term[13:0]	out	14-bit signed P component of PID controller

 The name of the file should be **P_term.sv**. The P_COEFF should be declared as a localparam and its value should be set to 5'h8. Keep in mind creating a signed multiply in verilog does not happen by default. To make a multiply signed both signals being multiplied have to be of type signed, and the result the product is assigned into has to be of type signed.



Write a test bench (*P_term_tb.v*) and instantiate the module. Apply several values to the inputs that would saturate both positive and negative and not saturate. The testbench should be self-checking.

Submit to the dropbox

- a) **P_term.sv**
- b) **P_term_tb.sv**
- c) **P_term_waves.png** (or JPG) that shows you simulated.

3) (20 pts)

No exercise for this problem...do on your own

- a. Below is the implementation of a D-latch.

```
module latch(d,clk,q);  
    input d, clk;  
    output reg q;  
  
    always @(clk)  
        if (clk)  
            q <= d;  
  
endmodule
```

Is this code correct? If so why does it correctly infer and model a latch? If not, what is wrong with it?


Submit to the dropbox a single file called HW2_prob4.sv

- a. The comments should answer the questions about the latch posed above.
- b. The file should contain the model of a D-FF with an active low synchronous reset.
- c. The file should contain the model of a D-FF with asynchronous active low reset and an active high enable.
- d. The file should contain the model of a SR FF with **active low asynchronous** reset. SR meaning it has a S input that will set the flop, and a R input that will reset the flop, and it maintains state if neither S or R are high. It also has active low async reset. This is a handy style flop that we will use frequently.
- e. I would like you to use the **always_ff** construct of System Verilog. The file should contain (as comments) the answer to this question: Does the use of the **always_ff** construct ensure the logic will infer a flop? Looking for a little more than a simple yes/no answer

This problem started as in class exercise (Ex08) on Mon Sept 27th

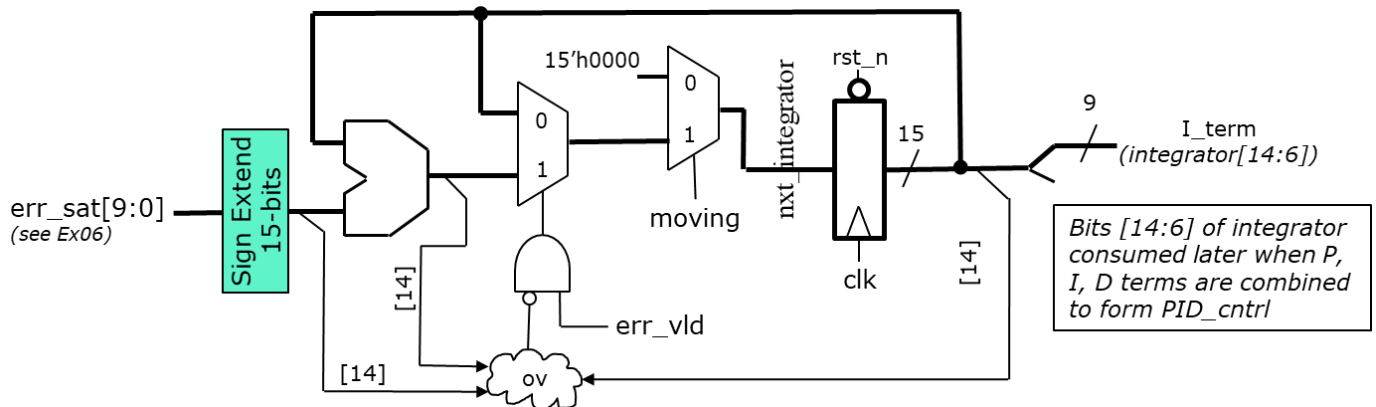4) (25 pts) I_term_DP.sv

See Exercise08 for more detailed description.



Signal:	Dir:	Description:
clk, rst_n	in	System clock and asynch active low reset
err_vld	in	A new error signal is valid and should be accumulated into I_term
moving	in	The Knight is moving so PID should be active
err_sat[9:0]	in	The error of the course (heading – desired_heading)
I_term[8:0]	out	The I_term for eventual use in PID control

Submit to the dropbox

- I_term.sv**
- I_term_tb.sv**
- I_term_waves.png** (or JPG) that shows you simulated.

This problem started as in class exercise (Ex09) on Fri Oct 1st

5) (35 pts) PWM11 & mtr_drv

See Exercise09 for detailed description.

Submit to the dropbox

- a) PWM11.sv
- b) PWM11_tb.sv
- c) Screen grabs of waveforms or some proof you actually ran your testbench
- d) MtrDrv.sv
- e) MtrDrv_tb.sv
- f) Screen grabs of waveforms or some proof you actually ran your testbench.