

ECE 551

HW3


- Due Mon Oct 18th @ 11:55PM
- Work Individually
- Remember What You Learned From the Cummings SNUG paper
- Use descriptive signal names and comment your code

HW3 Problem 1 (15pts) SM Design

Not Started as Exercise...you are on your own for this one.

A Single Slope A2D converter (capable of averaging 8 samples) was discussed in Lecture1. The block diagram is shown below. On the course webpage under HW3 you will find files:

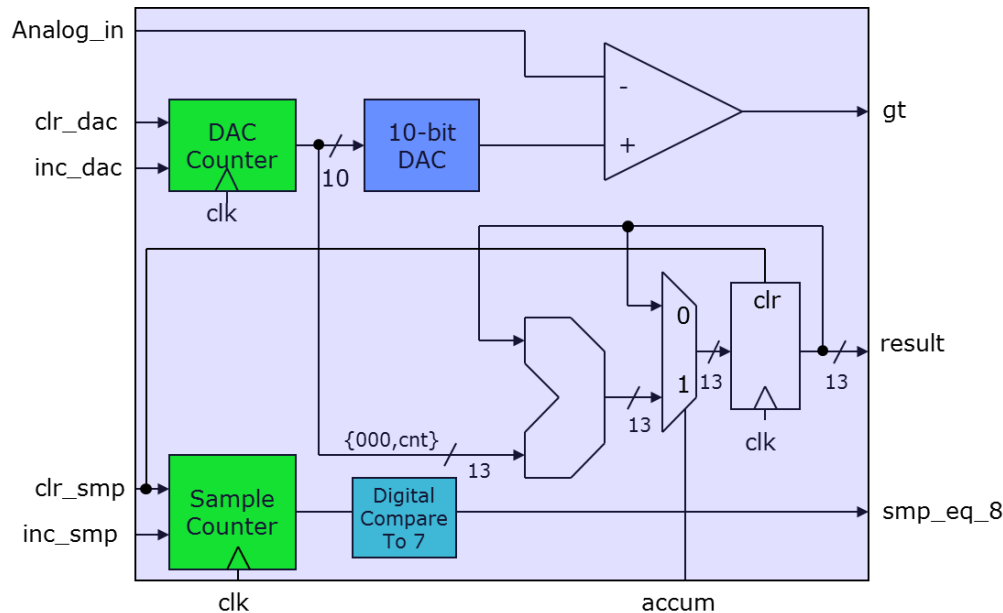ss_A2D_tb.v, **ss_A2D.v**, **ss_A2D_datapath.v**, **ss_A2D_SM_shell.sv**.



Flesh out **ss_A2D_SM_shell.sv** to complete the control (state machine). Simulate your resulting design using the provided self checking test bench. Submit your verilog for the state machine (file should be called **ss_A2D_SM.sv** to the dropbox for HW3). Also submit proof that it worked.

Recall there is a video in week1 (SS_A2D) that discusses this design.

HW3 Problem 2 (25pts) Signed Divider

Started as Ex11 on Fri Oct 8th


A brute force way to do division is count how many times you can subtract the divisor from the dividend.

A more elegant and efficient way would be to first start with the divisor shifted left $N-1$ bits and then see if it can be subtracted from the dividend. If so set the MSB of the quotient, shift the divisor right 1-bit and test for the next bit... For simplicity we will, not do this and rather just count how many time the non-scaled divisor can be subtracted from the dividend.

However, I don't want the problem to be too simple, so we will add some complexity by making this a signed divider.

The easiest way to accomplish this is to perform the actual division on the absolute values of the dividend & divisor and then negate the result if either the dividend xor the divisor was negative.

HW3 Problem 2 (25pts) Signed Divider

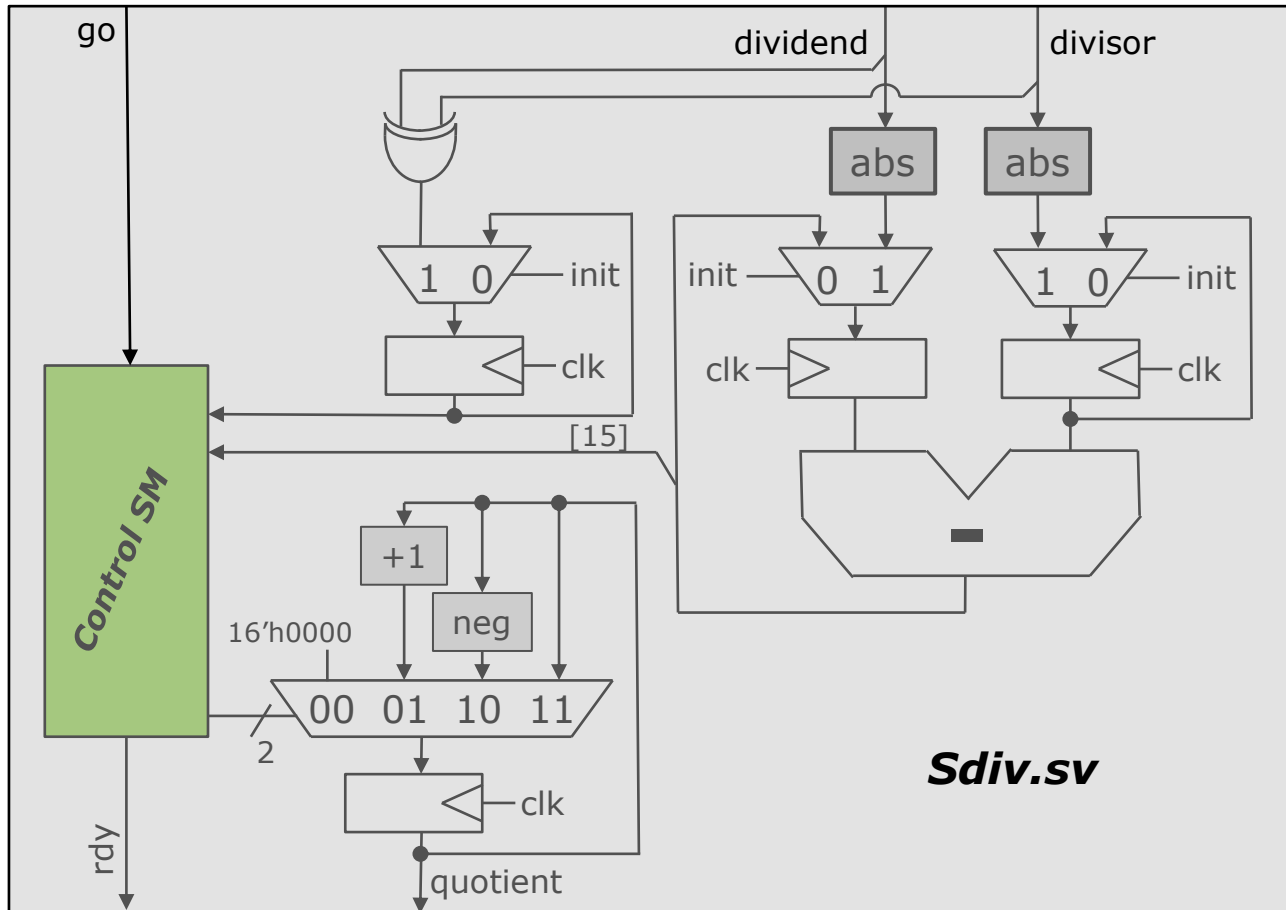


Study this proposed implementation of a signed divider then implement it in verilog. A high level (or one clock cycle pulse) on **go** initiates a divide. When the quotient is correct **rdy** should be asserted. **rdy** should stay high until the next time **go** is asserted (use a SR flop to implement **rdy**)

Create a testbench (**SDiv_tb.sv**) and test it with ++, +-, -+, and -- values of dividend and divisor. Testbench should be self checking.

Submit: SDiv.sv, SDiv_tb.sv, and proof your self-checking testbench ran.


What is UART (RS-232)

 - RS-232 signal phases
 - Idle
 - Start bit
 - Data (8-data for our project)
 - Parity (no parity for our project)
 - Stop bit – channel returns to idle condition
 - Idle or Start next frame




- Receiver monitors for falling edge of Start bit. Counts off 1.5 bit times and starts shifting (right shifting since LSB is first) data into a register.
- Transmitter sits idle till told to transmit. Then will shift out a 9-bit (start bit appended) register at the baud rate interval.

UART Receiver/Transmitter

 

A host computer will send commands to the Logic Analyzer via a UART serial peripheral


Signal:	Dir:	Description
clk,rst_n	in	50MHz system clock & active low reset
RX	in	Serial data carrying command from host computer
rdy	out	Asserted when a byte has been received
cmd[7:0]	out	Byte received (serves as command to LA)
clr_rdy	in	Asserted to knock down the rdy signal.

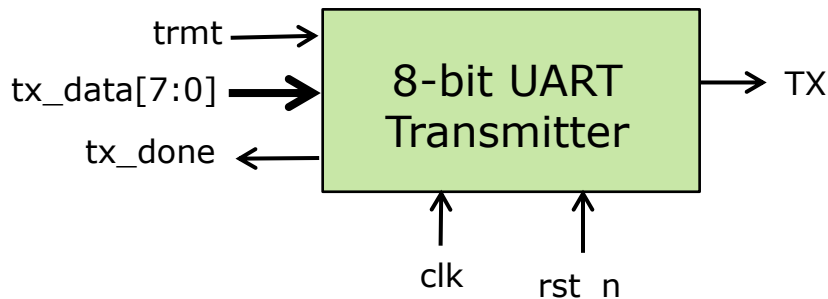

The follower sends responses back to the host computer. These responses are sent via a UART serial peripheral.

Signal:	Dir:	Description
clk,rst_n	in	50MHz system clock & active low reset
TX	out	Serial data output back to host
trmt	in	Asserted for 1 clock to initiate transmission
tx_data[7:0]	in	Byte to transmit (response from LA)
tx_done	out	Asserted when byte is done transmitting. Stays high till next byte transmitted.

Possible Topology of UART_tx

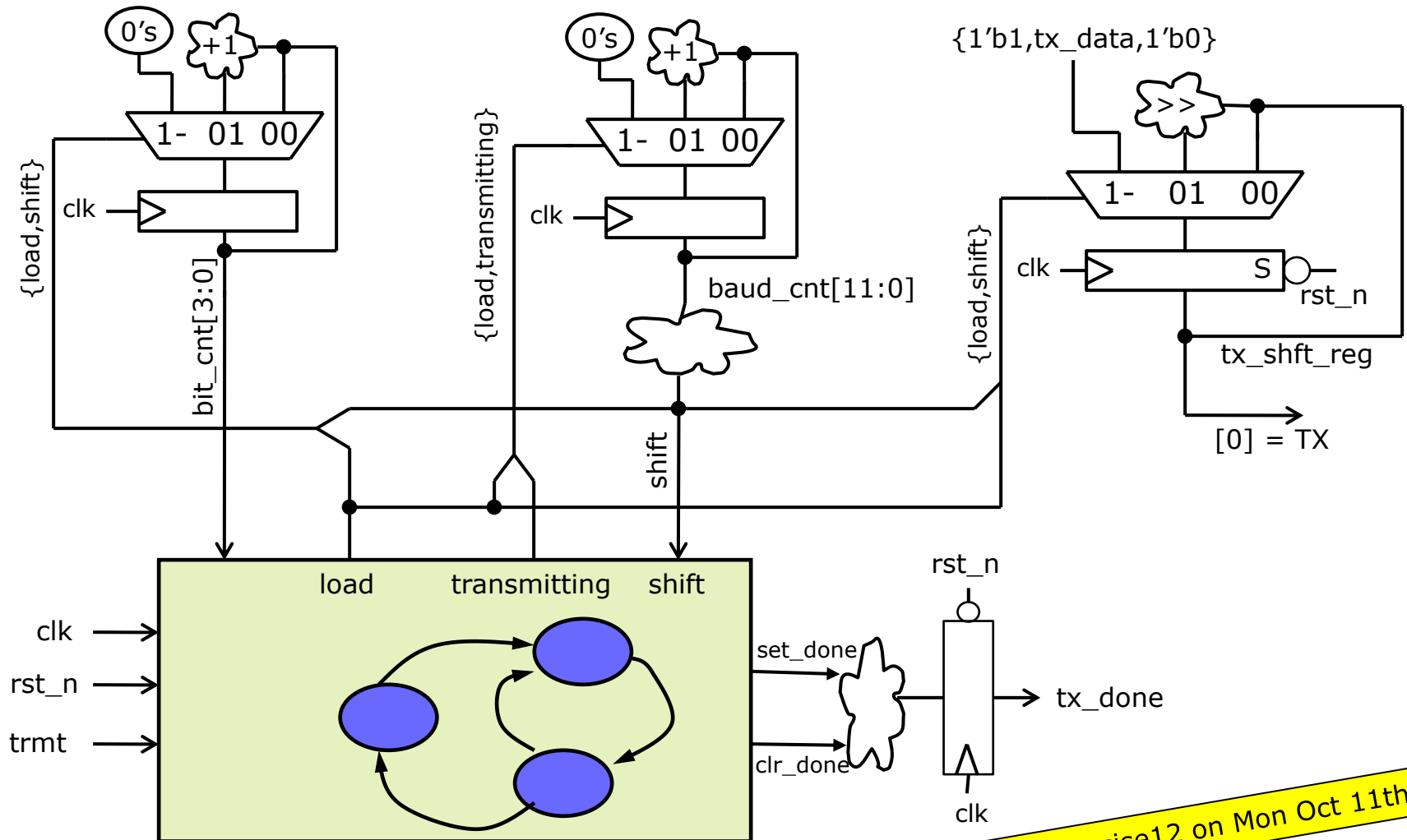

Started as Exercise12 on Mon Oct 11th

HW3 Problem 3 (20pts) UART Transmitter

Started as Exercise12 on Mon Oct 11th

Implement a the UART Transmitter (**UART_tx.sv**).

Make a simple test bench for it. This is one instance in which I would not spend too much time on the test bench. You can just instantiate your transmitter and send a few bytes. Verify the correct functionality (including baud rate) by staring at the green waveforms. You will make a more comprehensive test bench in the next problem.

Submit **UART_tx.sv** to the dropbox for HW3.


HW3 Problem 4 (20pts + 10pts) UART Receiver

Started as Exercise13 on Weds Oct 13th

Implement a the UART Receiver (**UART_rx.sv**).

Since you have a transmitter too, it is now easy to make a self checking test bench. Architect the test bench as shown. Is does the 8-bit value you transmit match the value you receive when the transmission completes.

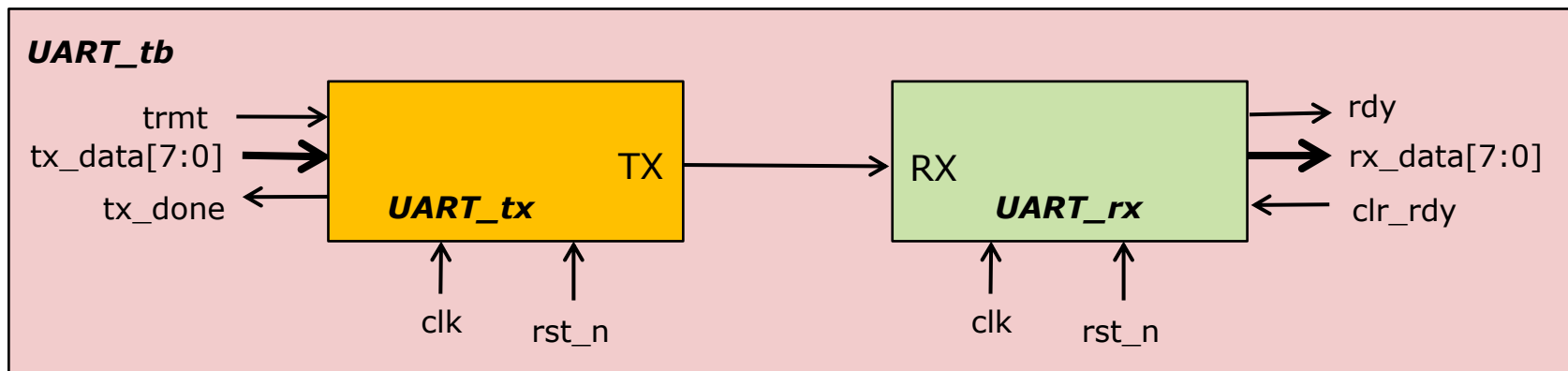Submit **UART_rx.sv** and your self-checking test bench (and **proof** it ran) to the dropbox for HW3.




HW3 Problem 5 (10pts) D_term of PID

Started as Exercise10 on Wed Oct 6th

The derivative of a function can be approximated by: $\frac{dF(t)}{dt} = \frac{f(t) - f(t - \Delta t)}{\Delta t}$

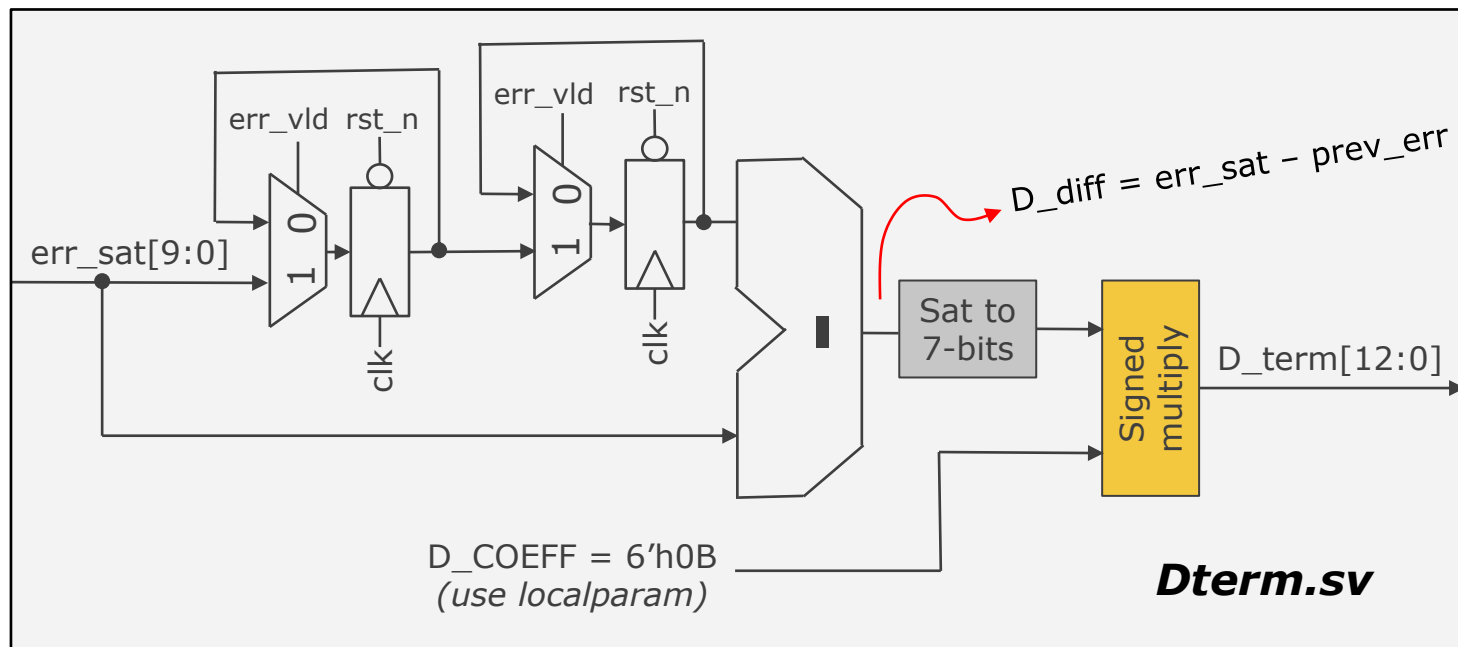We only need something proportional to the derivative so the divide by Δt is unnecessary. Consider the following circuit:



Submit: Dterm.sv, Dterm_tb.sv, and proof it ran.